
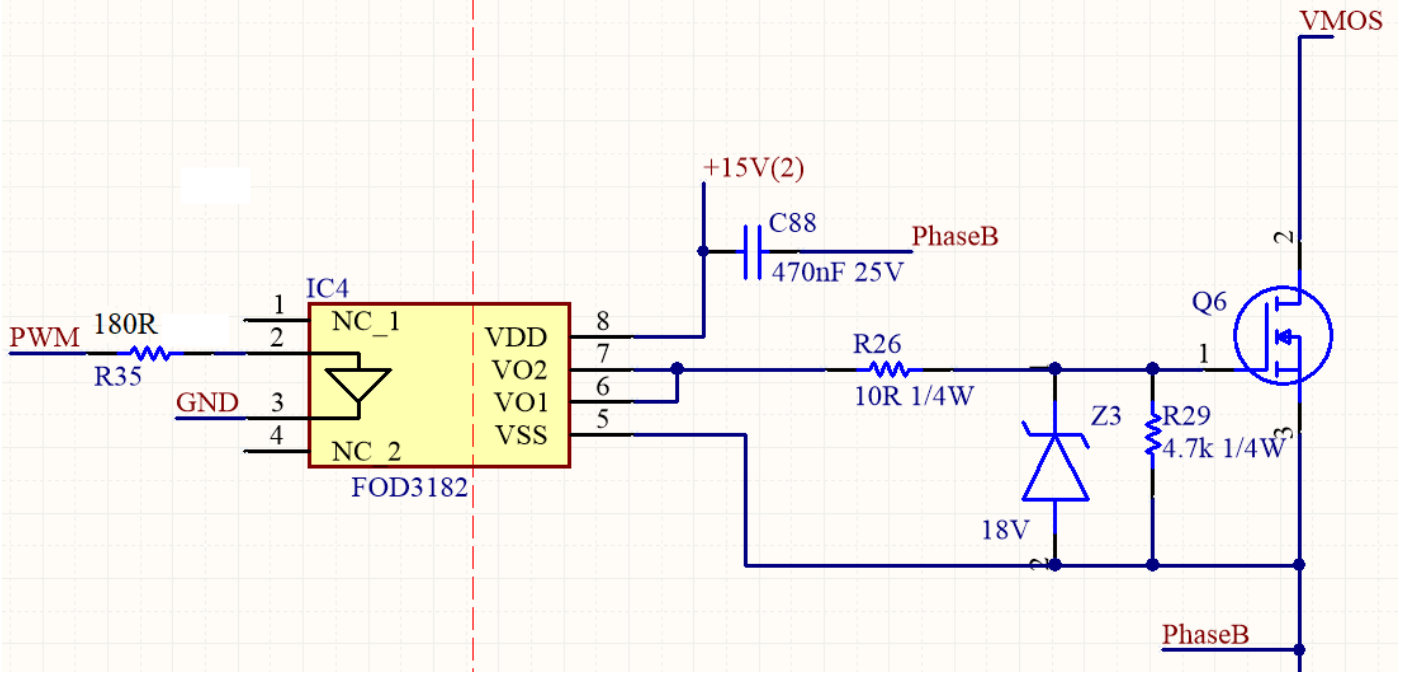


## OPTOLU SÜRME

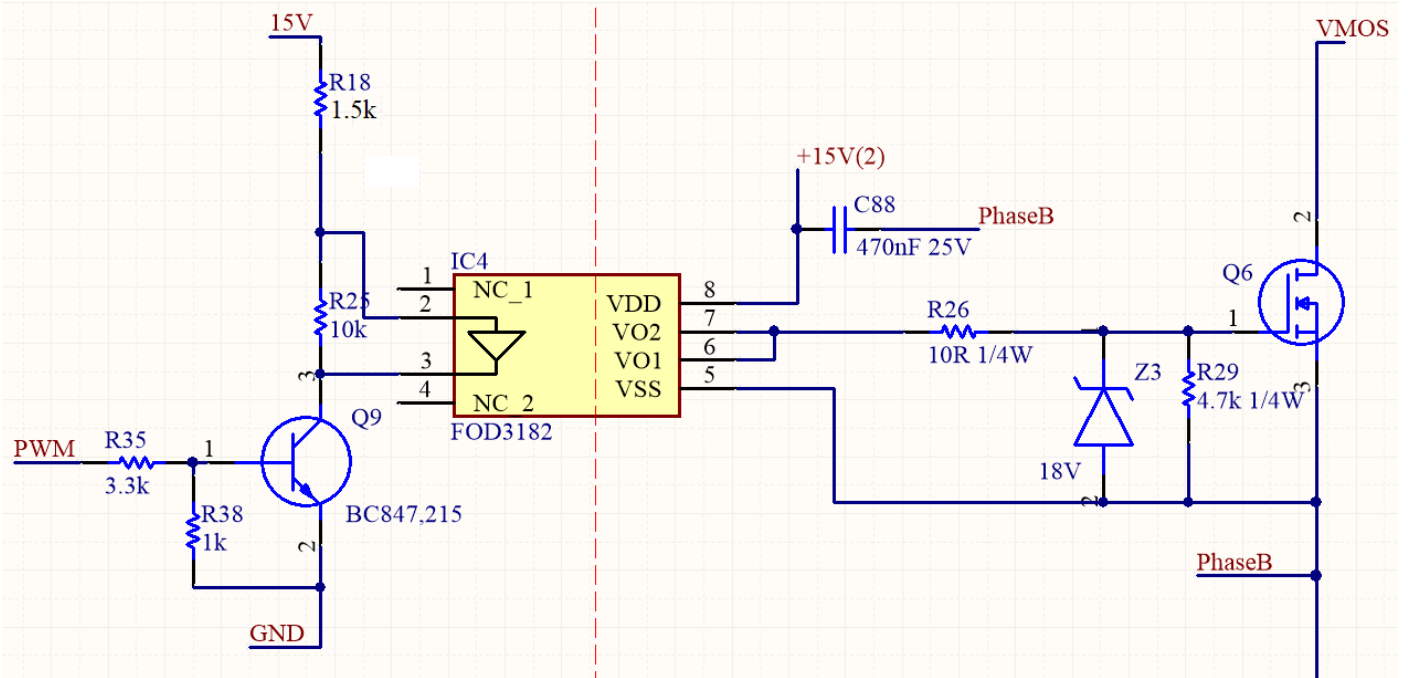

Şekil 1



Şekil 2

### Dezavantajları

- Yüksek sürme akımı
- İzoleli sürme gerilimi ihtiyacı
- Maliyet

### Avantajları

- PCB tasarımını açısından kolay uygulanabilir.
- İzolasyon
- Doluluk oranı (D) 1 olabilir.



$V_s$  pininin negatife düşme ihtimali

Max. doluluk oranı (D) sınırlı.



PCB tasarımı açısından uygulaması daha zor.

İzolasyon yok.



—

Maliyeti düşük.
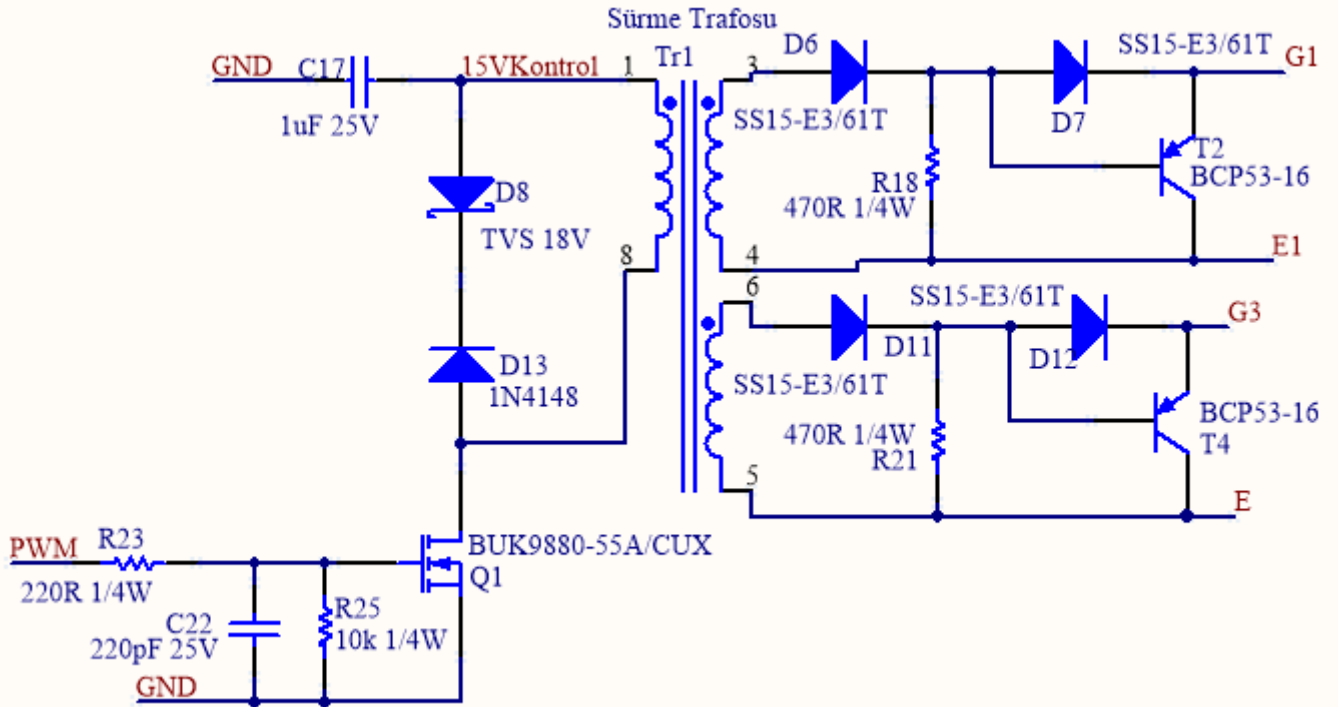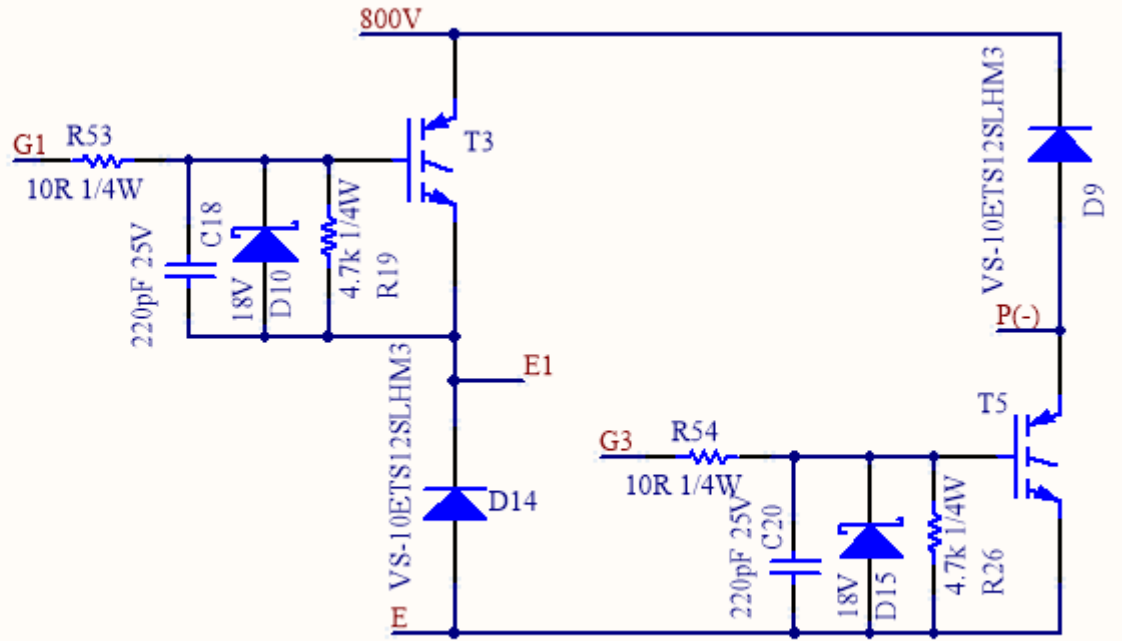
## Trafolu Sürme (2 Anahtarlı İleri Yönlü Dönüştürücü)


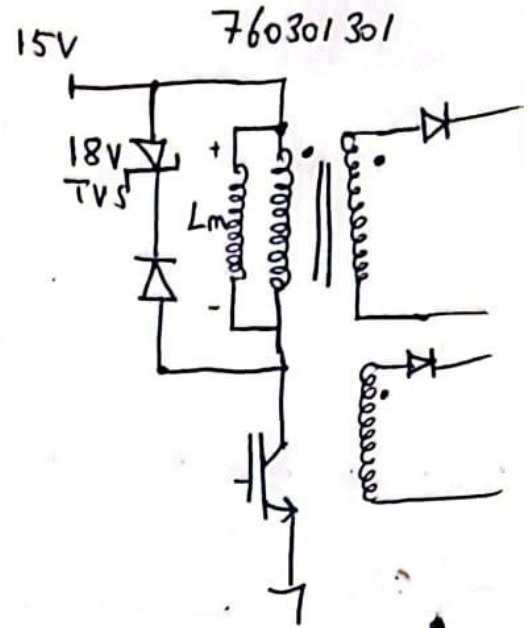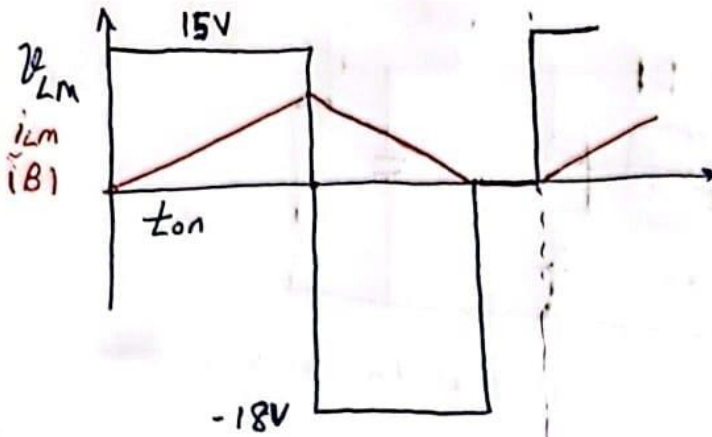
## #2 Anahtarlı FW Dönüştürücü Şürme Trafosu #



$$D_{max} = 0.15 \quad f = 100 \text{ kHz} \quad L_m = 750 \mu\text{H} \therefore$$

$$t_{on(max)} = 5 \mu\text{s} \quad i_{Lm(peak)} = \frac{15}{750 \mu\text{H}} \cdot 5 \mu\text{s} = 0.1 \text{ A}$$

$$P_{(TVS)} = 100 \cdot 10^3 \cdot \frac{1}{2} \cdot 750 \mu\text{H} \cdot (0.1)^2 = 0.375 \text{ W}$$

SMBJ18A uygun

$$V_{off-\mu s} = 15 \cdot 5 \mu\text{s} = 75 \text{ V}\mu\text{s}$$

(Trafonun izolasyon durumuna da dikkat)

izolasyon mesafesini arttırdım.

$$Nüve \Rightarrow \text{EF20} \quad A_e = 32.2 \text{ mm}^2 \quad A_L = 1540 \text{ nH/N}^2 \quad A_w = 61.8 \text{ mm}^2$$


- Doyum açısından

$$N \cdot \frac{d\phi}{dt} = V \Rightarrow N \cdot d\phi = V \cdot dt \Rightarrow N \cdot \Delta\phi = V \cdot \Delta t \Rightarrow N \cdot \Delta B \cdot A_e = V \cdot t_{on}$$

$$\Rightarrow N \cdot 0.25 \cdot 32.2 \cdot 10^{-6} = 15 \cdot 5 \mu\text{s} \Rightarrow N = 9.3 \Rightarrow N = 10$$

- Endüksiyon açısından.

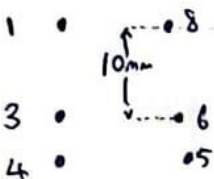
$$N^2 \cdot A_L = N^2 \cdot 1540 = 750 \mu\text{H} \Rightarrow N = 22 \quad \underline{N=22} \text{ seçtim}$$



$$\phi = 0.25 \text{ mm}$$



$$A_{cu} = \left( \frac{0.25^2}{2} \right) \cdot \pi = 0.05 \text{ mm}^2$$
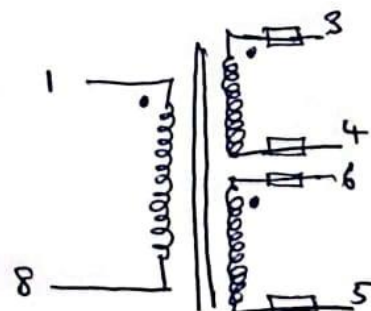
$$3 \times 22 \times 0.05 \text{ mm}^2 = 3.3 \text{ mm}^2$$





$$\frac{3.3}{61.8} = 0.05 \text{ mm}^2 \text{ rahat sığar.}$$
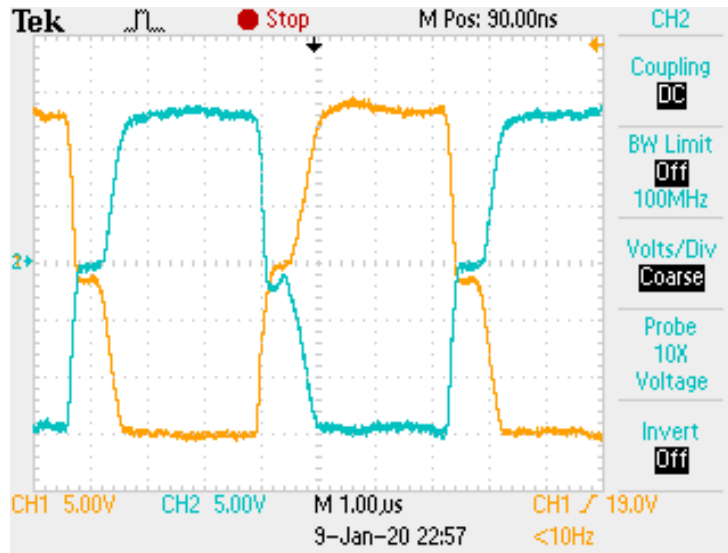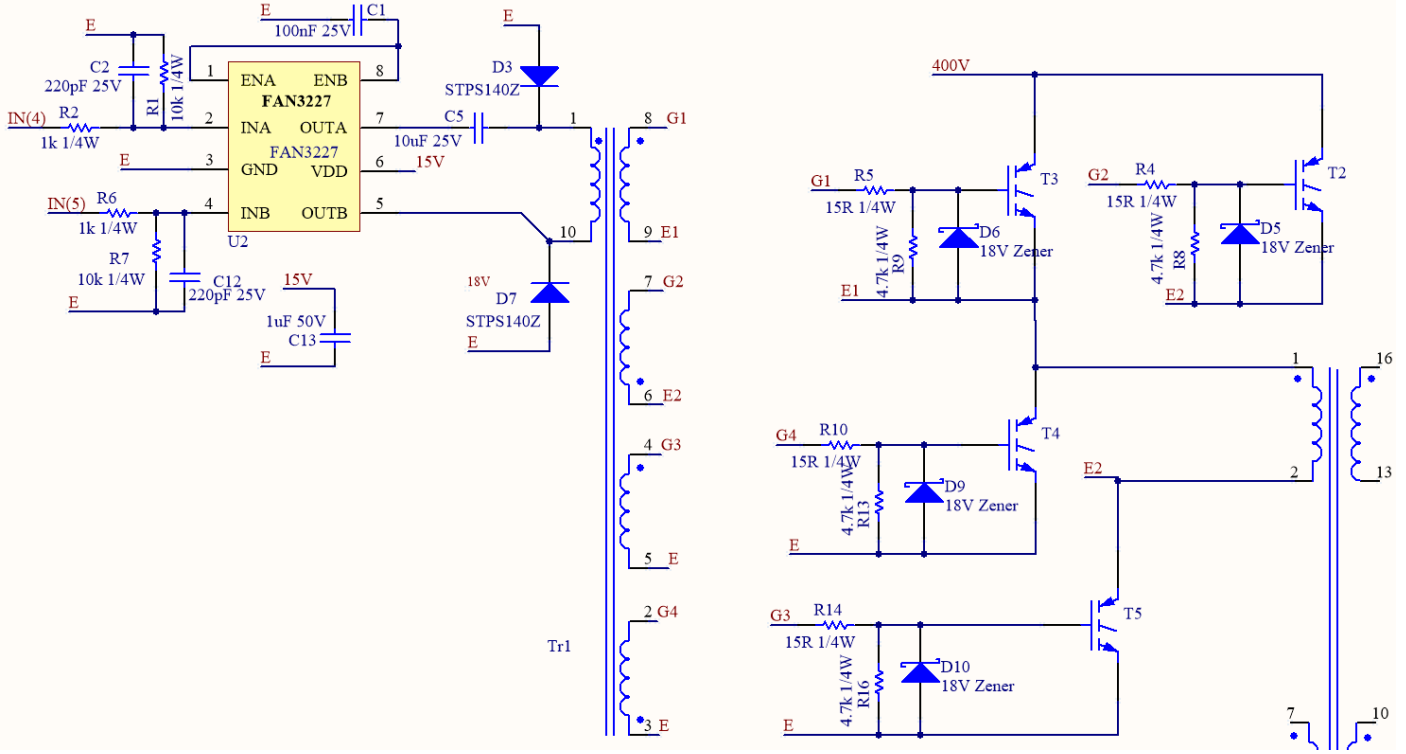
## Tam Köprü – Yarım Köprü Trafolu Sürme (1)



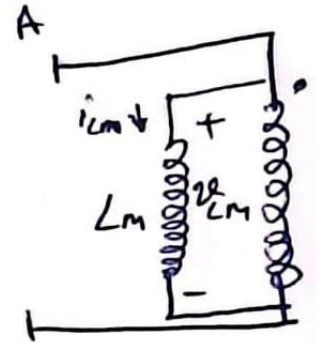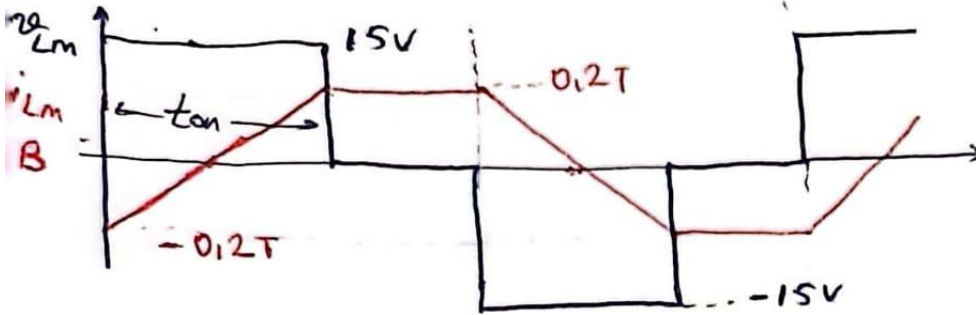
# Yarım Köprü – Tam Köprü Dönüştürücü Sürme Trafosu #




$$f = 100 \text{ kHz} \quad t_{on(max)} = 5 \mu s$$

$$N \cdot \Delta B \cdot A_e = V \cdot t_{on} \Rightarrow N \cdot 0.4 T \cdot A_e = 15 \cdot 5 \mu s \Rightarrow N \text{ bulunur}$$


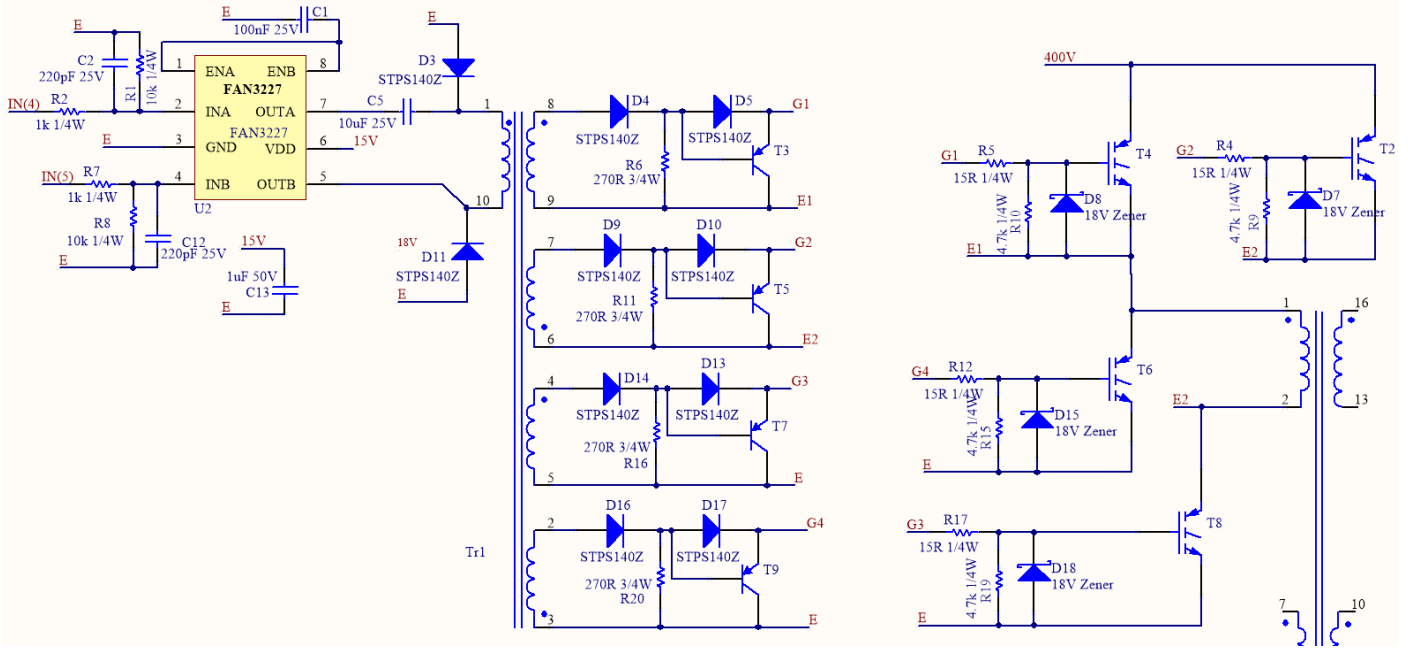
## Tam Köprü – Yarım Köprü Trafolu Sürme (2)




## Tam Köprü – Yarım Köprü Trafolu Sürme (3)

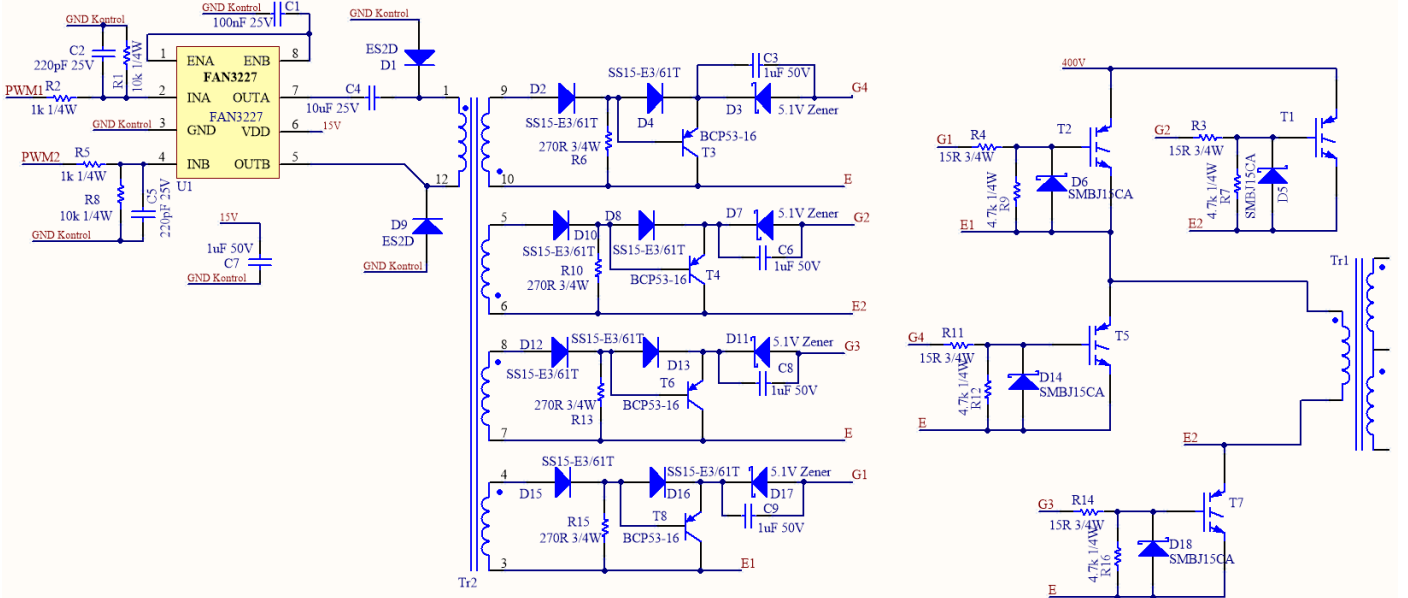


Trafo 1:1.5:1.5

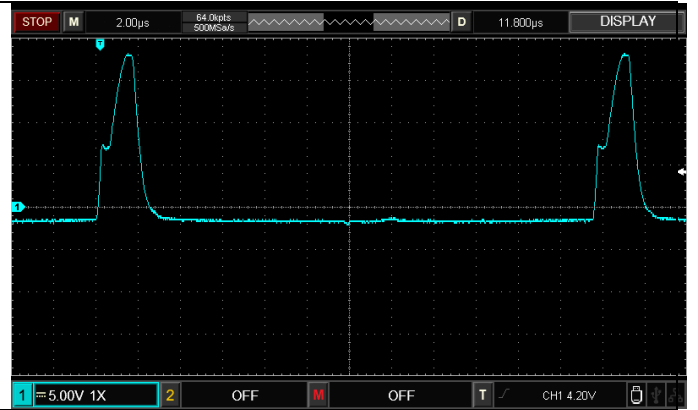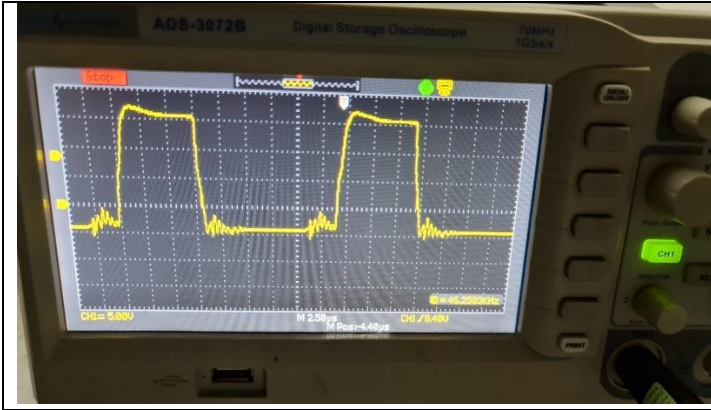
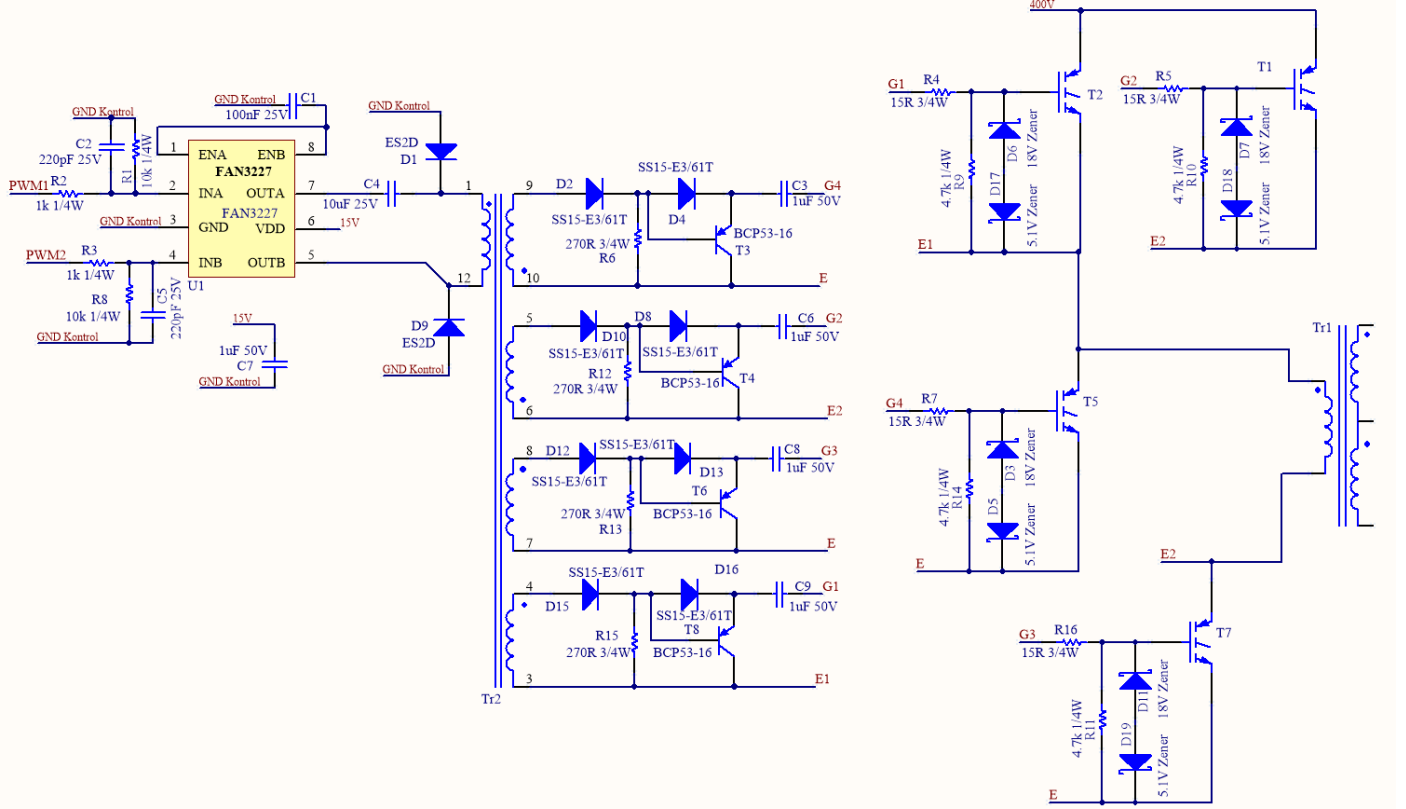
## Tam Köprü – Yarım Köprü Trafolu Sürme (4)




## Köprü – Yarım Köprü Trafolu Sürme (5)

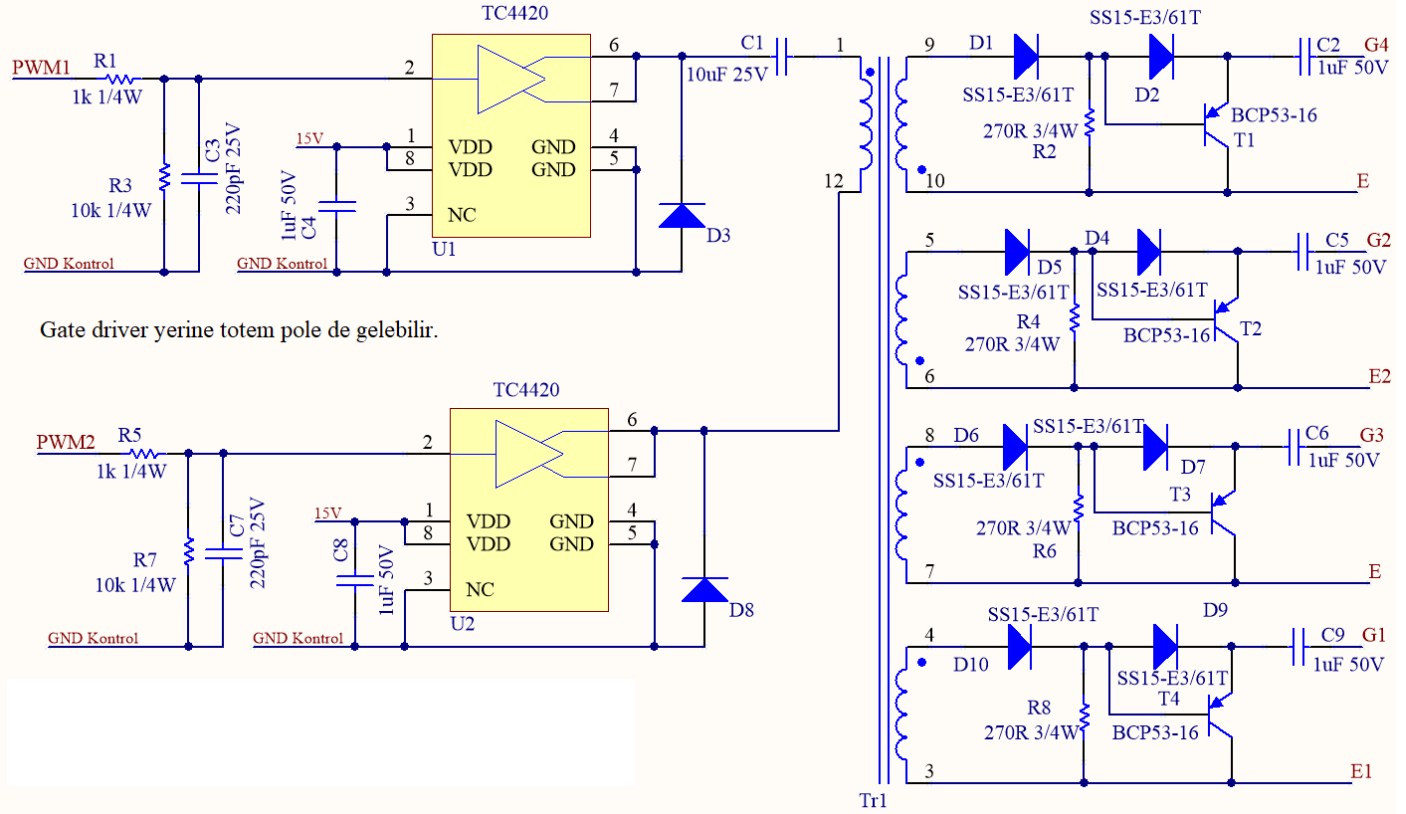




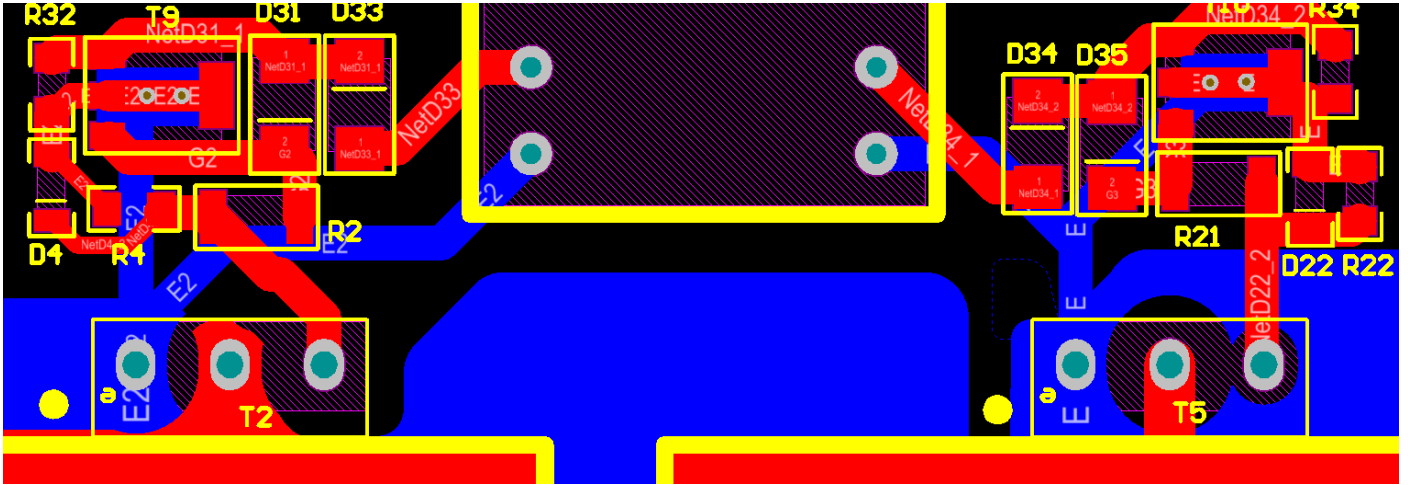İzoleli gerilim kaynağına ihtiyaç duymaz.



Trafo primer-sekonder parazitik kondansatöründen dolayı yüksek  $dv/dt$ 'li uygulamalarda (SiC gibi) gürültü problemi oluşabilir. (Common mode transient immunity düşük)

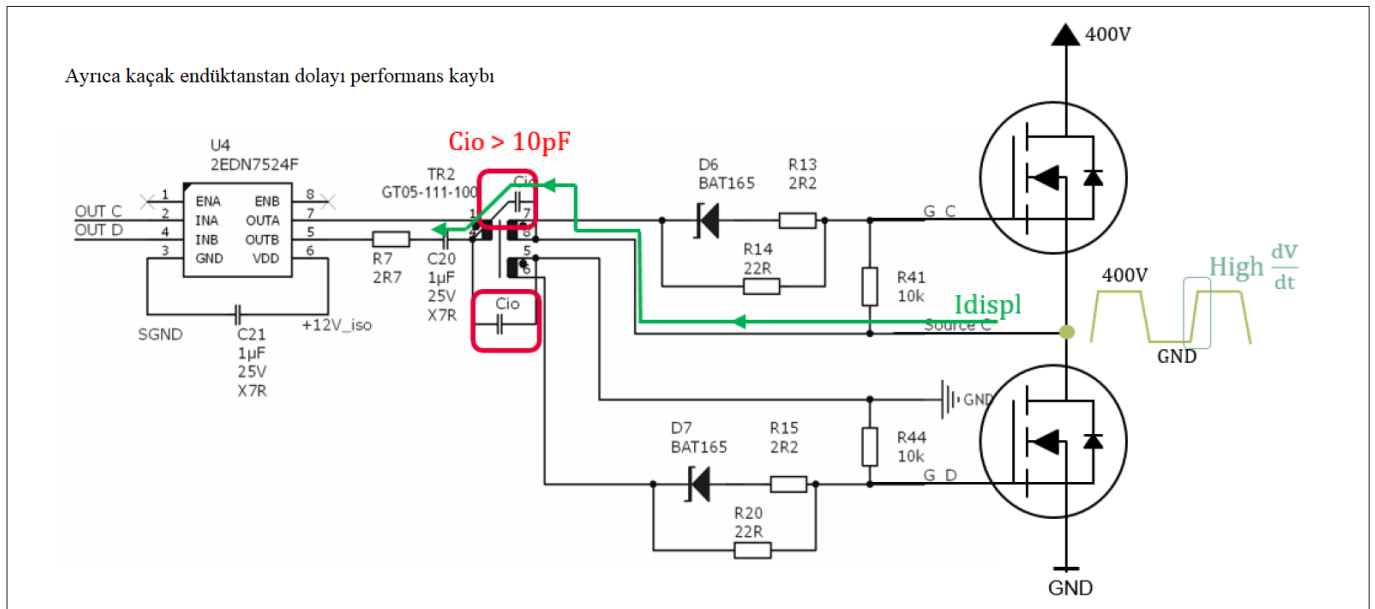
V/ns. Therefore, the use of pulse transformers is limited to applications with relatively slow voltage transients.



Ayrıca kaçak endüktanstan dolayı performans kaybı






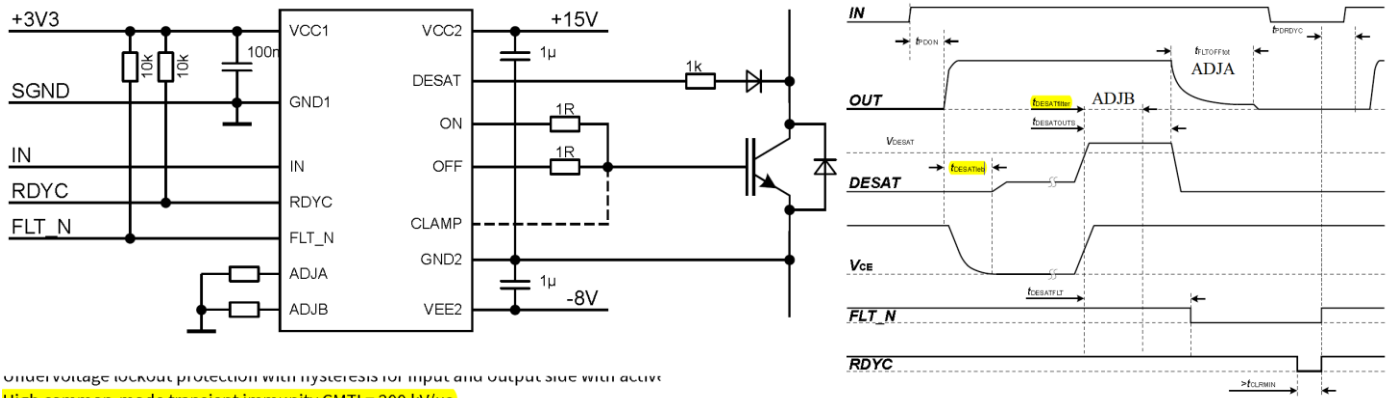
## SiC Örnek Bir Sürücü 1ED3461MU12MXUMA1





High common-mode transient immunity CMTI = 200 kV/μs


## COMMON MODE TRANSIENT IMMUNITY

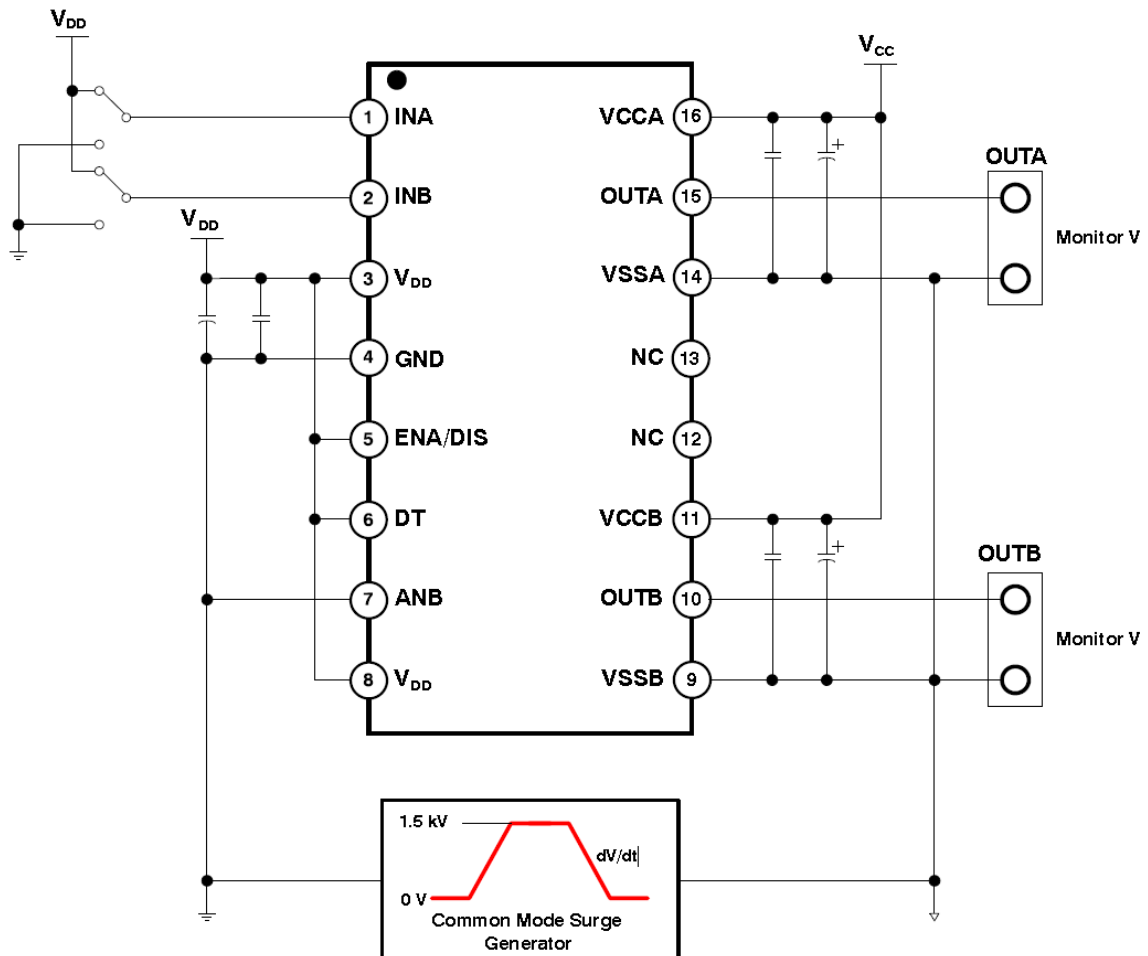

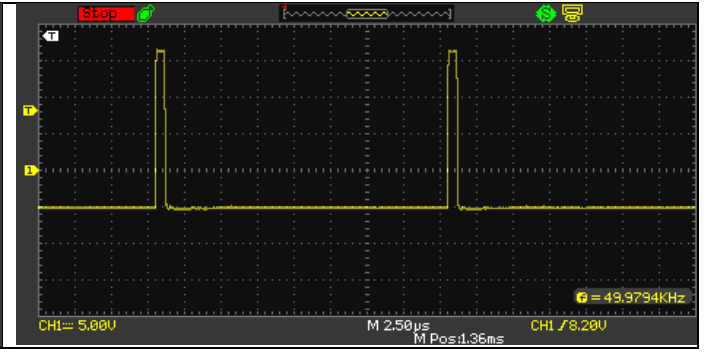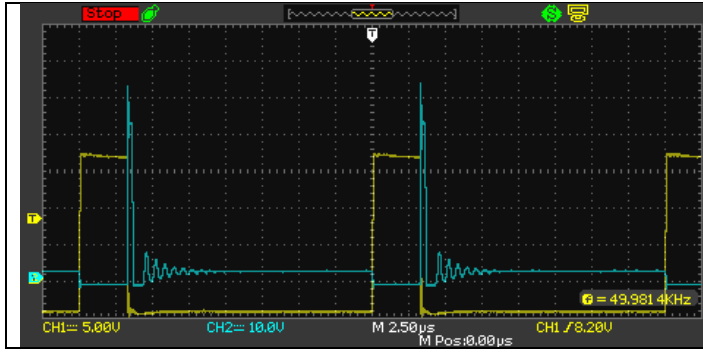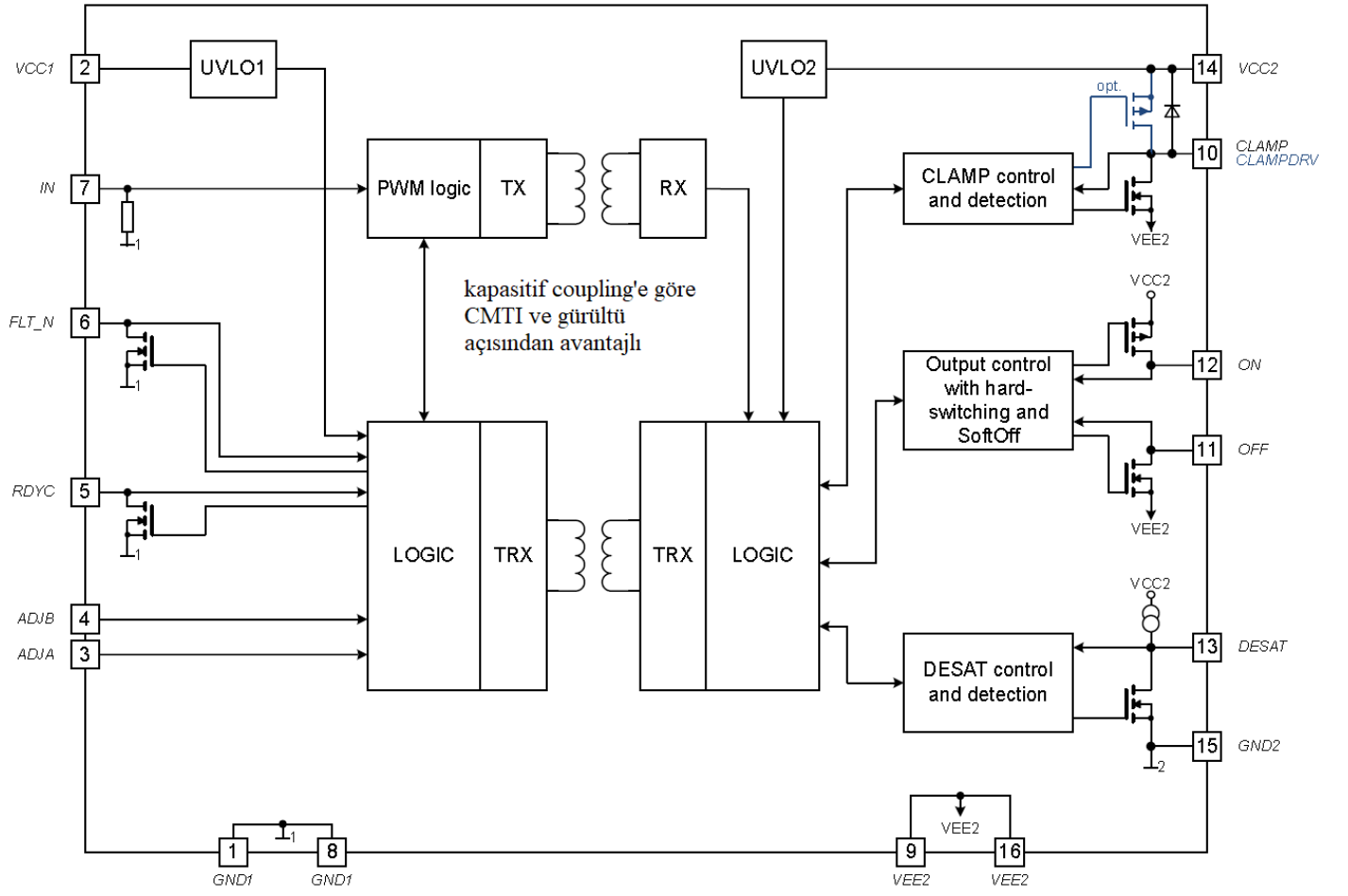


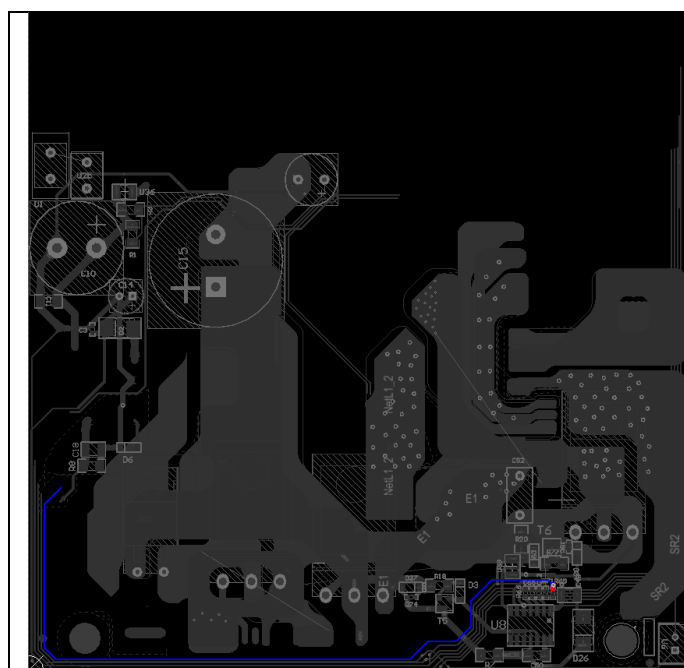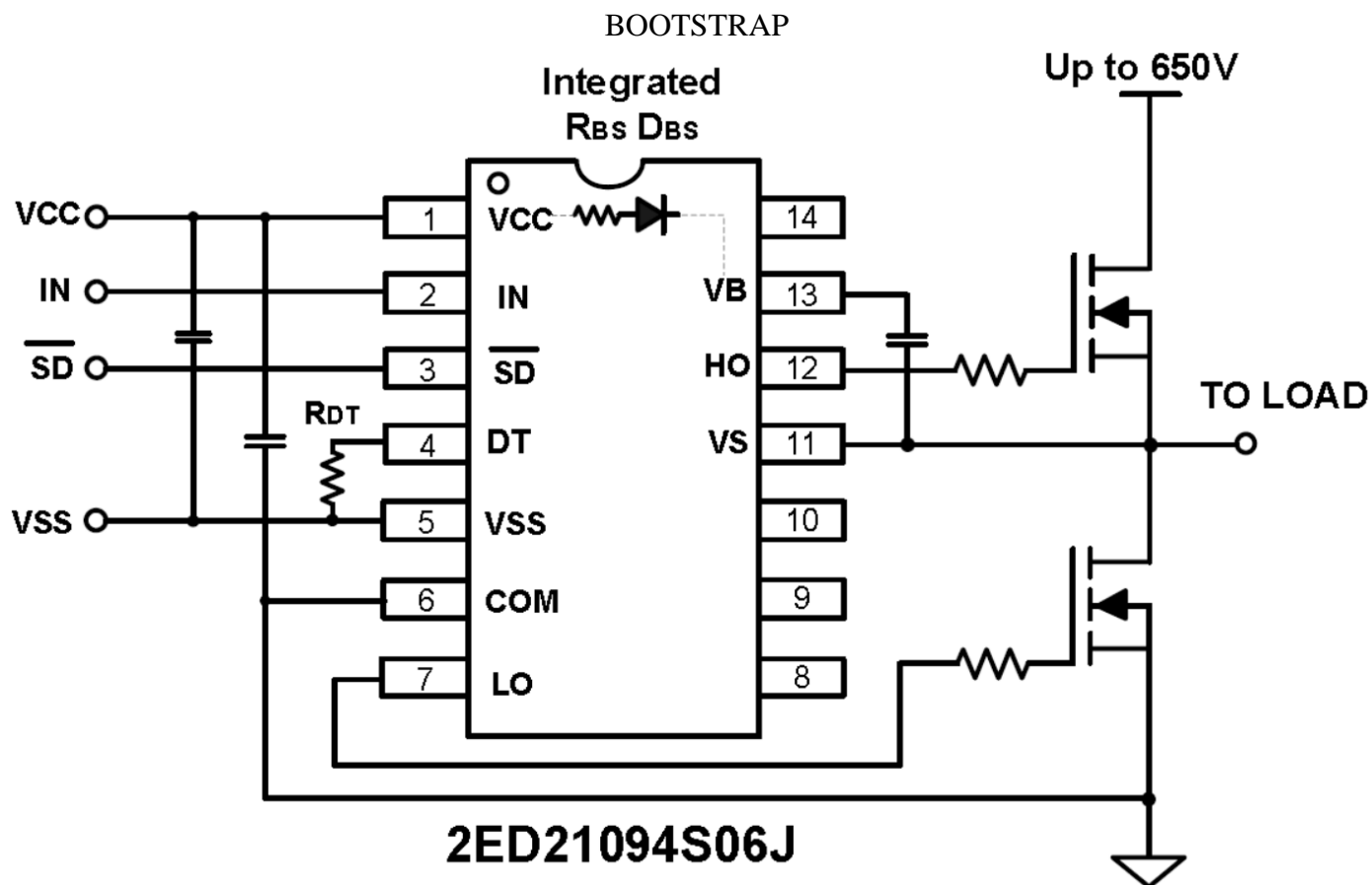


IN

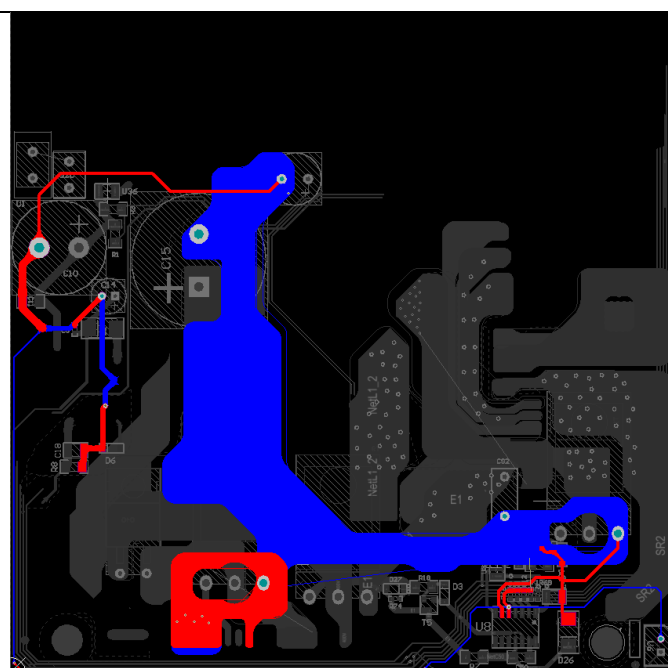


E

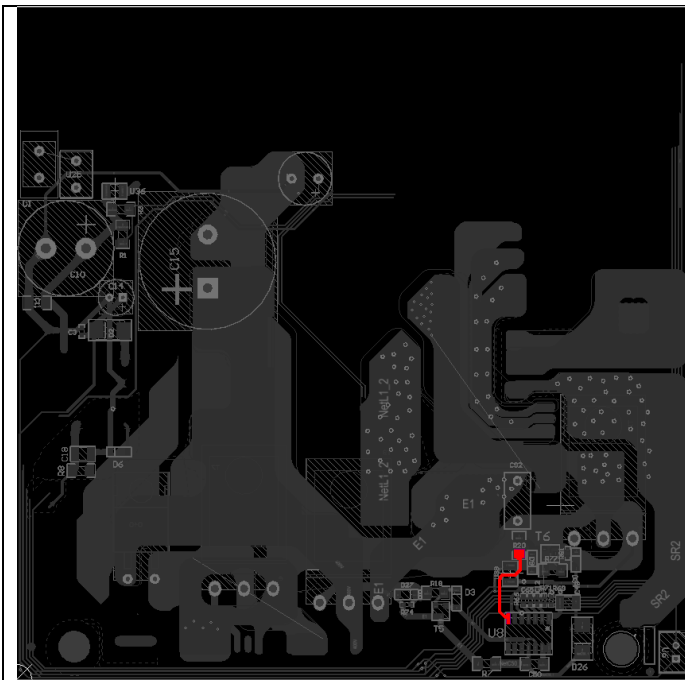


Sürme LO

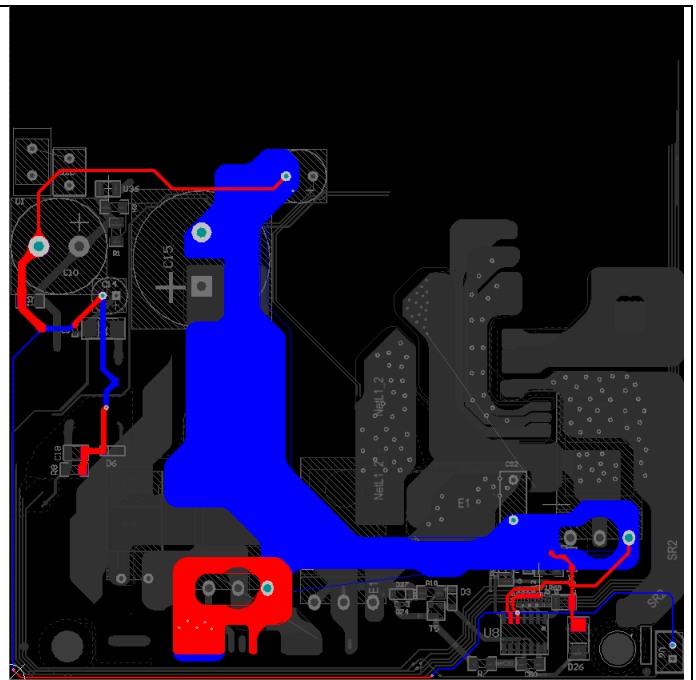

E (COM)

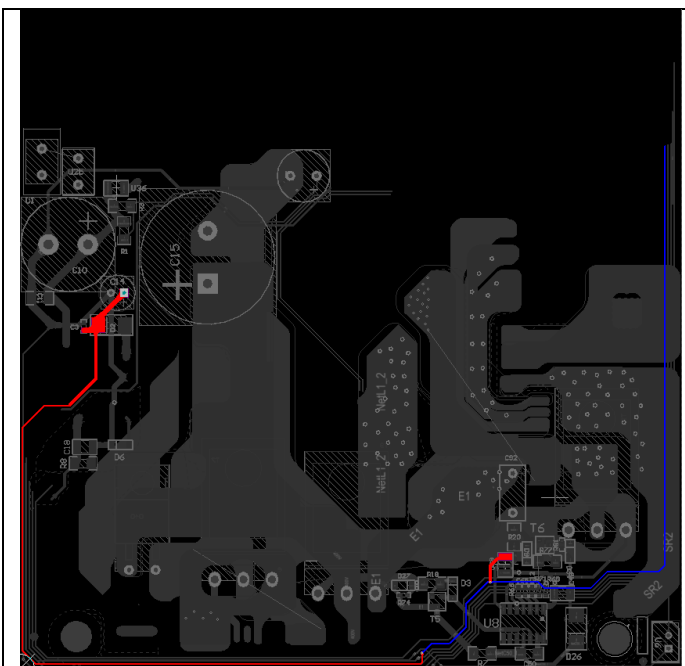

18V

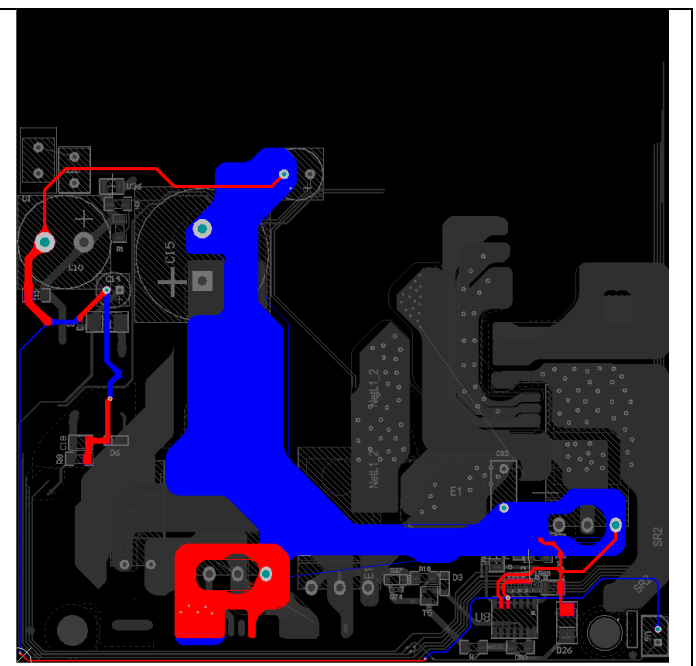

E (COM)

## 5.10 Tolerant to negative transients on input pins

Typically the driver's ground pin is connected close to the source pin of the MOSFET or IGBT. The microcontroller which sends the IN and /SD PWM signals refers to the same ground and in most cases there will be an offset voltage between the microcontroller ground pin and driver ground because of ground bounce. **The 2ED210x family can handle negative voltage spikes up to 5 V.** The recommended operating level is at negative 4 V with absolute maximum of negative 5 V. Standard half bridge or high-side/low-side gate drivers only allow negative voltage levels down to -0.3 V. **The 2ED210x family has much better noise immunity capability on the input pins.**

